

RAMAKRISHNA MISSION VIDYAMANDIRA

(Residential Autonomous College affiliated to University of Calcutta)

B.A./B.Sc. THIRD SEMESTER EXAMINATION, MARCH 2021

SECOND YEAR [BATCH 2019-22]

COMPUTER SCIENCE [GENERAL]

Date : 20/03/2021

Time : 11.00 am – 1.00 pm

Paper : III

Full Marks : 50

Answer **any five** questions from the following :

[5×10]

1. a) Perform the 2's complement subtraction of 11010-1101

b) Using De'Morgans theorem, show that $\overline{(A+B)}\overline{(A+B)} = 0$

[5+5]

2. a) Write the difference between primary memory and secondary memory?

b) Write down the difference between SRAM and DRAM

[5+5]

3. a) Discuss the Von Neuman architecture.

b) Discuss the Cache memory organization.

[5+5]

4. a) Briefly discuss the Hamming code error detection and correction technique with an example.

b) What do you mean by parity in context of error detection?

[5+5]

5. a) Design a combinational circuit that compares two 4-bit numbers A and B to check if they are equal. The circuit has one output x, so that $x = 1$ if $A = B$ and $x = 0$ if $A \neq B$.

b) A combinational circuit is defined by the following three Boolean functions. Design the circuit with a decoder and external gates.

$$F_1 = x'y'z' + xz, F_2 = xy'z' + x'y, F_3 = x'y'z + xy$$

[5+5]

6. a) Simplify the following Boolean function using four-variable map:

$$F(A, B, C, D) = \sum(0, 2, 4, 5, 6, 7, 8, 10, 13, 15)$$

b) Implement Full-Adder using NOR gates.

c) Define “prime implicant” and “essential prime implicant”.

[3+5+2]

7. a) How Race around condition or limitation of JK flip flop get eliminated?

b) How do you convert a JK flip-flop to a T flip-flop?

[5+5]

8. a) Design a binary up counter.

b) What is counter?

[5+5]

_____ × _____