

RAMAKRISHNA MISSION VIDYAMANDIRA

(Residential Autonomous College affiliated to University of Calcutta)

B.A./B.Sc. THIRD SEMESTER EXAMINATION, MARCH 2021

SECOND YEAR [BATCH 2019-22]

ELECTRONICS [GENERAL]

Date : 20/03/2021

Time : 11.00 am – 1.00 pm

Paper : III


Full Marks : 50

Answer **any five** questions from the following :


[5×10]

1. a) KCL and KVL are alternate statements for conservation of charge and conservation of energy respectively. Explain it.

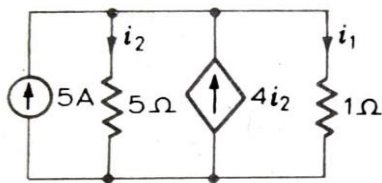b) Find the currents i_1 and i_2 in the following circuit:




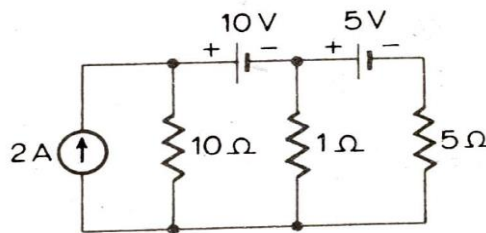c) Calculate the current and power drop in the resistance 5Ω of the following circuit:




[(1.5+1.5)+3+4]

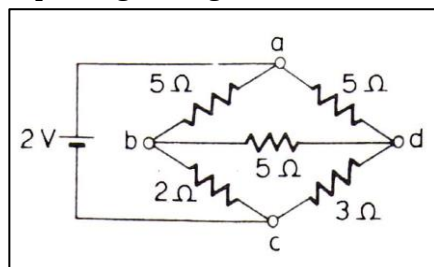2. a) Find the current passing through the 2V source in the following circuit:




b) State and explain Superposition theory.

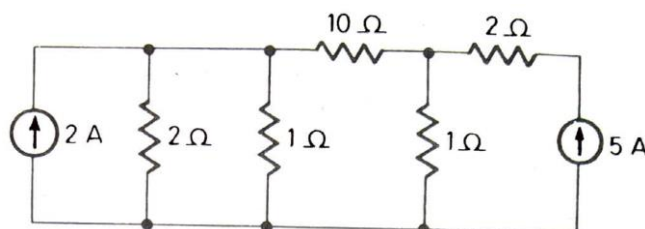c) Use Thevenin's theorem to determine the power loss across the 10Ω resistance in the following circuit:



[3+(1+2)+4]

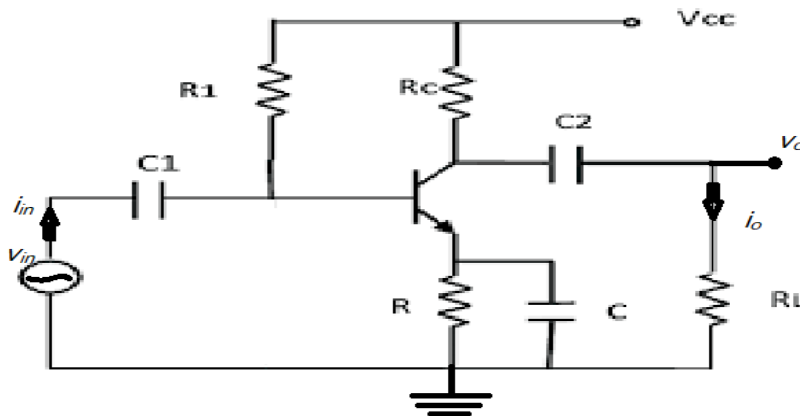3. a) Mention two applications for negative and positive feedback respectively.
 b) State and explain Barkhausen criteria for sustained oscillation.
 c) Draw a Wien-Bridge oscillator circuit. Obtain expression for frequency of oscillation of that circuit. For a Wien-Bridge oscillator if the frequency determining resistance and capacitance values are $R = 1\text{ K}\Omega$ and $C = 0.1\text{ }\mu\text{F}$, then calculate the frequency of oscillation. [2+2+(1+3+2)]
4. a) Compare JFET and MOSFET. Draw the cross-sectional diagram of a JFET at pinch-off and beyond pinch-off respectively.
 b) Explain how a Depletion type MOS can be used as an Enhancement type MOS. Draw a CMOS device and mention all the layers in the diagram.
 c) For a FET device the *trans-conductance* is 10 mA/V and *channel resistance* is $0.1\text{ M}\Omega$. Find the value of *amplification factor* of the device. [(2+2)+(2+2)+2]
5. All the hydride parameters are standard of the following circuit. Find (a) input impedance (b) output impedance (c) current gain and (d) voltage gain



[2+2+3+3]

6. a) Find the relation between α and β of a transistor.
 b) Using the KVL, and KCL explain the CE configuration of an NPN transistor.
 c) How many classes of the amplifier are there? Explain any two. [2+4+4]
7. a) Design a 6 V full-wave circuit with a shunt C-filter.
 b) Draw circuits for CB and CC configuration using NPN transistor. [6+4]
8. Write short notes on any four of the following: [4×2.5]
 a) Reciprocity theorem
 c) Uni-Junction Transistor
 d) Pinch-off in FET
 e) Avalanche Breakdown
 f) Load line

_____ × _____