

RAMAKRISHNA MISSION VIDYAMANDIRA

(Residential Autonomous College affiliated to University of Calcutta)

B.A./B.Sc. THIRD SEMESTER EXAMINATION, MARCH 2021

SECOND YEAR [BATCH 2019-22]

PHYSICS (HONOURS)

Paper : V [CC 5]

Date : 12/03/2021

Time : 11 am - 1 pm


Full Marks : 50

Answer any five questions:

[5 × 10]

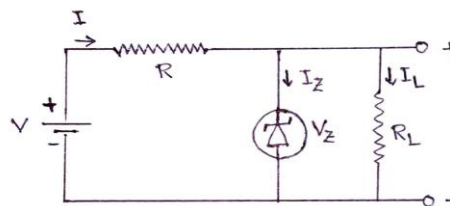1. a) How does the depletion region form in a PN junction diode?
b) In a PN junction diode, draw the schematic diagram for the following:
 - i) Electric field variation
 - ii) Variation of electro-static potential
 - iii) Electron energy variation
 - iv) Energy band diagram in unbiased conditionc) In a diode rectifier without filter the load resistance $R_L = 1000 \Omega$, supply voltage $V_S = 311.\sin(314t)$ volts and the source resistance $R_S = 50 \Omega$. Determine (i) the DC component of load voltage, (b) the peak instantaneous diode current and (c) the peak inverse voltage across the diode.

[2+(1+1+1+2)+(1+1+1)]
2. a) What is the difference between Avalanche breakdown and Zener breakdown of a PN junction diode?
b) Mention the comparisons between ordinary semiconductor diode and Zener diode.
c) In the following circuit the source voltage V is 12 volts and the voltage across the Zener diode V_Z is 9 volts. The maximum and minimum allowable Zener currents are 4 mA and 40 mA respectively. Find the value of the resistance R . Find also the range of allowable values of the resistance R_L .




- d) Why is Bridge rectifier superior than centre tapped full-wave rectifier?


[1.5+1.5+(2+3)+2]
3. a) What do you mean by pinch-off in a FET? Draw the schematic of cross-section of a depletion type MOSFET at pinch-off and beyond pinch-off respectively.
b) Compare enhancement type and depletion type MOSFET. Explain how a Depletion type MOS can be used as an Enhancement type MOS.
c) In a common-source JFET amplifier the load resistance $R_L = 500 \text{ k}\Omega$. Assume $g_m = 0.2 \text{ mA/V}$ and $r_d = 100 \text{ k}\Omega$. Calculate the voltage gain of the amplifier.

[(1+2)+(2+1)+4]
4. a) Draw the energy variation curve for an open-circuited n-p-n transistor. How is the curve modified when the transistor is operating in the active region?
b) A p-n-p transistor working in the CB mode has an input dynamic resistance of 50Ω . The current gain of the amplifier is 0.98 and the load resistance in the collector circuit is $3 \text{ k}\Omega$. Calculate the voltage gain and the power gain.

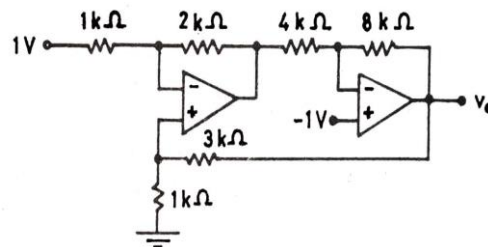- c) For a CE configuration, it is found that for a fixed base current of $30 \mu\text{A}$, collector current changes from 3.5 mA to 3.7 mA when collector-emitter voltage changes from 7.5 V to 12.5 V . Calculate its output resistance and β at 12.5 V . [(1.5+1.5)+3+4]
5. a) What do you mean by distortions in amplifiers? Discuss the origin of the input and the output nonlinear distortions in transistor amplifiers. What is the desired position of the Q-point for a minimum distortion and why?
- b) A CE amplifier has a load resistance of $5 \text{ k}\Omega$ and an unbypassed 100Ω resistor in the emitter lead. The h -parameters are: $h_{ie} = 5000 \Omega$, $h_{re} = 7.5 \times 10^{-4}$, $h_{fe} = 150$ and $h_{oe} = 30 \mu\text{A/V}$. Determine the current gain, the input resistance, the output resistance and the voltage gain.
- c) What is the need of cascading of amplifiers? Obtain overall voltage gain of a cascaded system of n number of amplifiers. [(1+2+1.5)+3+(1+1.5)]
6. a) Draw the circuit diagram of a two stage RC coupled CE amplifier. Show how the magnitude and phase angle of its voltage gain vary with frequency. Qualitatively explain these variations.
- b) An RC coupled amplifier has a mid-frequency gain of 100. The gain is 80 at 50 Hz and 100 Hz. Calculate the half-power frequencies.
- c) Show that the negative feedback in an amplifier can reduce (i) phase distortion and (ii) frequency distortion. [(1+1+2)+3+(1.5+1.5)]
7. a) Compare Colpitts, Hartley and Crystal oscillator.
- b) A Wien Bridge oscillator is to be operated in the frequency range 30 Hz to 3 KHz. The variable capacitance has a range 50 pF to 500 pF. Find the resistance values required. If the resistances in the other arms are in the 5:1 ratio, then find out the required gain of the amplifier.
- c) What is multivibrator? Describe the operation of a multivibrator with circuit diagram, that can produce clock pulses. How do you control the time period of these clock pulses? [3+3+(0.5+3+0.5)]
8. a) Find out the output voltage v_o in the following circuit:



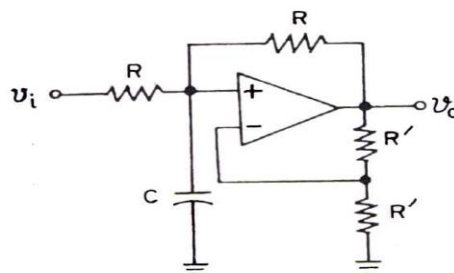- b) For the following circuit derive an expression of the output voltage v_o in terms of the input voltage v_i . What is the function of the circuit?



- c) What is DAC? Describe the working principle of a R-2R ladder type DAC. [3+3+(0.5+3.5)]

_____ × _____