

RAMAKRISHNA MISSION VIDYAMANDIRA

(Residential Autonomous College affiliated to University of Calcutta)

B.A./B.Sc. FIFTH SEMESTER EXAMINATION, FEBRUARY 2022

THIRD YEAR [BATCH 2019-22]

COMPUTER SCIENCE (HONOURS)

PAPER : XII [CC12]

Date : 28/02/2022

Time : 11 am – 1 pm

Full Marks : 50

Answer **any five** of the following questions:

[5×10]

1. a) The barrier potential across a p-n junction diode cannot be measured by placing a voltmeter across the diode terminals. Explain the reason in brief.
- b) What is breakdown diode? Discuss how breakdown takes place across the junction of a diode.
- c) Derive expressions for DC value of load current and ripple factor for a bridge rectifier.
- d) A bridge rectifier is connected to a load resistance of 5 k Ω . At the input of the rectifier an unregulated power supply of 100 Volt (rms) is connected. Each diode of the rectifier has a forward resistance of 50 Ω . Calculate the DC load voltage and the ripple factor at the output.

[2+(1+2)+(1+2)+2]

2. a) Define the factors α and β for a bipolar junction transistor. Establish a relation between them.
- b) A BJT is operating in the CE configuration and draws a constant base current I_B of 30 μ A. The collector current I_C is found to change from 3.5 mA to 3.7 mA when the collector-emitter voltage V_{CE} changes from 7.5 Volt to 12.5 Volt. Calculate the output resistance and β at $V_{CE} = 12.5$ Volt. What is the value of α ?
- c) What is thermal runaway? How can it be avoided using proper dc biasing of the BJT?
- d) Draw the h-parameter equivalent circuit of a single stage CE amplifier. Obtain expressions for input resistance and voltage gain for the CE the amplifier by using the h-parameters.

[(1+1) +3+ (1+1) + (1+2)]

3. a) A three stage amplifier is designed by connecting three amplifiers in series. All of them have voltage gain 2 but current gain 1, 2 and 5 respectively. An input signal of 10 mW is applied to the multistage amplifier. Find the output signal power.
- b) Why is feedback necessary in amplifiers? Obtain expression for gain in feedback amplifier. Explain under which condition it can be transformed into an oscillator.
- c) Draw and explain timing diagram of LXI H, 8050.

[2+3+5]

4. a) What is PSW?
- b) A main memory is specified as 4K \times 8. Indicate the number of words, word size and total capacity of this memory.
- c) How is RST 7.5 is different from other interrupt lines?

[3+4+3]

5. a) Compare addressing modes of 8086 with that of 8085.
- b) Describe different segment registers of 8086.

[6+4]

6. a) Calculate the physical address when the content of CS is C800H and content of IP is 1234H in 8086 system.
- b) Write an assembly language program in 8085 to add two 16-bit numbers. Also calculate the estimated time to execute the program if the clock frequency is 3.072 MHz. [3+7]
7. a) Write down the characteristics of embedded systems. Explain any two of those.
- b) What are the roles of '%assign' and '%equ' directives in x86 assembly language programming?
- c) Write down about various handshake signals for programmable peripherals. [4+3+3]

_____ × _____