

# RAMAKRISHNA MISSION VIDYAMANDIRA

(Residential Autonomous College under University of Calcutta)

B.A./B.SC. FIRST SEMESTER EXAMINATION, DECEMBER 2012

FIRST YEAR

COMPUTER SCIENCE (General)

Date : 21/12/2012

Time : 11 am – 1 pm

Paper : I

Full Marks : 50

## Group - A

(Answer **question no. 1** and **any two** from question 2 to 4)

1. Answer **any two** from the following: 2½x2
- a) There are two representation of zero in 1's complement"- comment on it with proper example. 2½
- b) Prove the Idempotent law in Boolean algebra. Write the Distributive law written for three variables. 1½+1
- c) i) Find the two number of 1, in the binary representation of  $8 \times 1024 + 3 \times 64 + 3$ . 1
- ii) Find the maxterm for the Boolean function  $F(x,y,z)=1$ . 1½
- d) Prove the following logical equation using Boolean algebra

$$(A + B + C)(B + AC) = BC + AC \quad \text{2½}$$

Answer **any two** questions from the following:

2. a) Prove that if  $xy=0$ , then  $x'y+xy'=x+y$ . 2½
- b) Convert the following to other canonical form 2½
- $$F(A, B, C) = \sum(1, 4, 5, 6, 7)$$
- c) Simplify the Boolean function using k map procedure-
- (i)  $F = \sum(1, 3, 7, 11, 15) + \sum_d(0, 2, 5)$
- (ii)  $F(w, x, y, z) = \sum(0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$  2½+2½=5

3. a) Compare and contrast between weighted code and nonweighted code. 2½
- b) List the Huntington postulates of Boolean algebra. 6
- c) Subtract  $(1010100)_2 - (1000100)_2$  using 1's complement arithmetic. 1½
4. a) Represent the decimal number "25" in (a) BCD code (b) Octal code (c) Gray code 1½x3
- b) Solve the equation for x 1½
- $$x_{16} = (1111111111111111)_2$$
- c) Apply DeMorgan's Theorem for the following expression  $\overline{(A + B + C)}D$  2½
- d) Find the 10's complement of  $(935)_{11}$  1½

## Group - B

(Answer **any two** from the following)

5. a) "A decoder may be called a minterm generator"- Comment on statement. 2½
- b) Give the functional truth table of a 4:1 multiplexer and realize it using basic gates AND, OR and NOT. 4
- c) What is code converter? Draw the logic diagram of BCD to excess 3 code converter. 4
- d) What are the advantages of using multiplexer? 2

6. a) Design a full subtractor circuit using minimum number of 2-input NAND gates. Write the Boolean function. 5
- b) Draw the truth table for a three input adder. Write down the truth table and Boolean expression for sum and carry. 5
- c) What is meant by a priority Encoder? How it is different from Encoder? 2½
7. a) Design a combinational circuit where output is equation to 1 if the input variables have more 1's than 0's. The output is 0 otherwise. 4
- b) Define excitation table? Derive the excitation table for R-S flip-flop. 1½+3
- c) Convert a SR flip-flap to a D flip-flop. 4
8. a) What do you mean by Race around condition? In which flip-flop does it occur? Give two solutions so that Race-condition will never occur (with suitable illustration and figures). 2+1½+7
- b) Design an asynchronous sequential circuit to realize a mod-4 up counter. 3

