

RAMAKRISHNA MISSION VIDYAMANDIRA

(Residential Autonomous College affiliated to University of Calcutta)

B.A./B.Sc. FIRST SEMESTER EXAMINATION, DECEMBER 2015

FIRST YEAR [BATCH 2015-18]

COMPUTER SCIENCE [Gen]

Date : 17/12/2015

Time : 11 am – 1 pm

Paper : I

Full Marks : 50

[Use a separate Answer Book for each group]

Group – A

Answer **any one** question :

1. a) What do you mean by self-complementary code? Explain with example. [2.5]
b) Convert $(FACE)_{16} = (?)_2 = (?)_8$ [2.5]
2. Explain the following terms with examples : [2×2.5]
 - a) Parity bit
 - b) De-morgan's theorem

Answer **any two** questions :

3. a) What are the unused bit combinations for excess-3 code? Give reasons. [2]
b) Determine the base of the numbers in the following operations : [1.5+1.5]
(i) $14/2 = 5$; (ii) $132 - 25 = 104$
c) Find the value of $25_{10} - 35_{10}$ using 1's complement and 2's complement method. [2]
d) The state of a 12-bit register is 100010010111. What is its content if it represents
 - i) three decimal digits in BCD?
 - ii) three decimal digits in 84 – 2 – 1 code? [1.5+1.5]
4. a) Without using truth table, prove that $\overline{(a + b)} = \bar{a} \cdot \bar{b}$. [2.5]
b) Explain Floating Point notation with an example. [3]
c) Show that a positive logic NAND gate is a negative logic NOR gate. [2]
d) To get the output value as same as the value of expression $\bar{a}bc + a\bar{b}c + ab\bar{c} + abc$ from a circuit for three inputs a, b, c, find the minimum number of different basic gates which you consider to form the circuit in minimum cost. Give reasons. [2.5]
5. a) Draw the circuit using only NOR gates for the following expression $(A + B)(C + D)E$. [3]
b) Simplify the following Boolean function by first finding the essential prime implicants :
 $F(A, B, C, D) = \sum(1, 3, 4, 5, 10, 11, 12, 13, 14, 15)$. [5]
c) What do you mean by odd function, explain with an example. [2]
6. a) For transmission of 6-bit message [1+2]
 - i) How many minimum number of parity bits be needed for only single bit error detection?
 - ii) How many parity bits be needed for single bit error detection and correction?
b) Describe the necessary steps to convert a 4-bit gray code to its binary equivalent with an example. [2.5]
c) Define Hamming Code and explain its use with example. [4.5]

Group – B

Answer **any one** question :

7. a) Write down the working principle of priority encoder. [2]
b) Convert a D Flip-flop into a JK Flip-Flop. [3]

8. a) How can a D flip flop be operated in toggle mode? [2]
 b) Derive the characteristic equation for J-K flip flop. [3]

Answer **any two** questions :

9. a) Design a 2-bit magnitude comparator. [3·5]
 b) 'A full adder is a combination of two half adders and one OR gate' — Justify. [2·5]
 c) Implement a BINARY to GRAY code converter. [4]
10. a) Convert the following to other canonical form : $F(A, B, C, D) = \sum(0, 2, 6, 11, 13, 14)$. [3]
 b) Implement a 4-to-16 decoder using two 3-to-8 decoders. [4]
 c) Prove that, NOR gate is universal. [3]
11. a) Simplify the expression $f = \Pi(1, 3, 5, 8, 9, 11, 15)$ using K-map. [6]
 b) Differentiate between asynchronous and synchronous counter. [2]
 c) 'A flip flop is a 1-bit memory element' —Justify. [2]
12. a) Design a 2-bit asynchronous up-down counter using T flip flop and explain its operation. [3+3]
 b) Differentiate between sequential and combinational logic circuit. [2]
 c) What is the difference between register and counter? [2]

————— × —————