

**RAMAKRISHNA MISSION VIDYAMANDIRA**  
(A Residential Autonomous College under University of Calcutta)

**First Year**

**First-Semester Examination, December 2010**

Date : 18-12-2010

**ELECTRONICS (General)**

Full Marks : 50

Time : 10am – 12noon

**Paper - I**

**Answer any five questions :**

[5×10 = 50]

1. a) Subtract decimal number 25 from 49 using 2's complement method.  
b) Starting from the expression  $Y = A'B + AB'$ , simplify it to draw the circuit by using NOR gates only.  
c) If the voltage measuring range of a digital voltmeter is 0 to 10V and 16 bit encoding is used, then what will be the resolution in voltage reading? [3+3+4 = 10]
2. a) Realize the function  $F = \sum m(0, 1, 4, 5, 7)$  using 4:1 MUX.  
b) Write the truth table of a full adder and draw the circuit by using NAND gates only.  
c) Convert the decimal number 156.7 into BCD. [4+4+2 = 10]
3. a) If  $X = ABC + AB'C' + A'BC'$  and  $Y = (A' + B' + C')(A' + B + C)(A + B' + C)$ ; then find the relation between X and Y?  
b) What is decoder? Explain the operation of BCD to binary decoder. [3+(2+5) = 10]
4. a) What is race-around problem for J-K flip-flop? How can it be avoided?  
b) Design a circuit that divides a clock to 1/8th of its initial frequency using J-K flip flops.  
c) State the difference between latches and flip flop. [(2+2)+3+3 = 10]
5. a) Design a counter that counts 0, 2, 4, 3, 9, 10, 13 in this order using all JK flip-flops. Explain the operation.  
b) What is shift register? Explain the operation of a 4-bit PISO shift register. [4+(2+4) = 10]
6. a) Define Fan-in and Fan-out in digital circuitry.  
b) How are the synchronous counters more advantageous than asynchronous counters? Explain.  
c) Design a 4:1 MUX using NAND gates only. [(1½×2)+5+2 = 10]
7. a) Design a 16:1 MUX using 4:1 MUXs and basic gates and explain the operation.  
b) Illustrate about different uses of MUX and DEMUX. [6+4 = 10]