

RAMAKRISHNA MISSION VIDYAMANDIRA

(Residential Autonomous College under University of Calcutta)

B.A./B.SC. SECOND SEMESTER EXAMINATION, MAY 2012

FIRST YEAR

ELECTRONICS (General)

Date : 28/05/2012

Time : 11 am – 1 pm

Paper : II

Full Marks : 50

Answer **any five** questions :

1. a) What do you mean by Fermi level? [2]
b) Show the position of Fermi level for intrinsic and extrinsic semiconductors. [3]
c) How does a semiconductor differ from a metal considering the energy band structure? [3]
d) State 'Mass-action' law. [2]
2. a) Describe how the barrier field is formed across a P-N junction. [5]
b) Can you measure the barrier potential with a voltmeter? Explain. [2]
c) Describe the origin of reverse saturation current in P-N diode. [3]
3. a) How does a photodiode work? [3]
b) How does a Zener diode act as a voltage regulator? [2]
c) Distinguish between Avalanche breakdown and Zener breakdown. [5]
4. a) Explain with a circuit diagram the operation of a full wave bridge rectifier. [2+4]
b) Define Ripple voltage and Ripple factor. [2+2]
5. a) Define α and β of a BJT and derive the relation between them. [1+1+1]
b) Draw the output characteristics of the CE mode for a BJT. Indicate the different regions on the characteristics. [2+2]
c) Derive the load-line for a CE amplifier and draw it on the output characteristics. [2+1]
6. a) 'BJT' is a current-controlled device but FET is a voltage controlled device' — Why? [3]
b) Distinguish between BJT and FET. [4]
c) Draw the transfer characteristics of a p-channel JFET. Define transconductance of a FET. [2+1]
7. a) Briefly describe the operation of an enhancement mode P-channel MOSFET. [5]
b) Derive the small signal ac equivalent circuit of a common-source FET amplifier. [5]

