

RAMAKRISHNA MISSION VIDYAMANDIRA

(Residential Autonomous College under University of Calcutta)

B.A./B.SC. THIRD SEMESTER EXAMINATION, DECEMBER 2013

SECOND YEAR

Electronics (General)

Paper : III

Date : 20/12/2013


Time : 11am – 1pm

Full Marks : 50

Answer **any five** of the following questions:

(5 × 10)

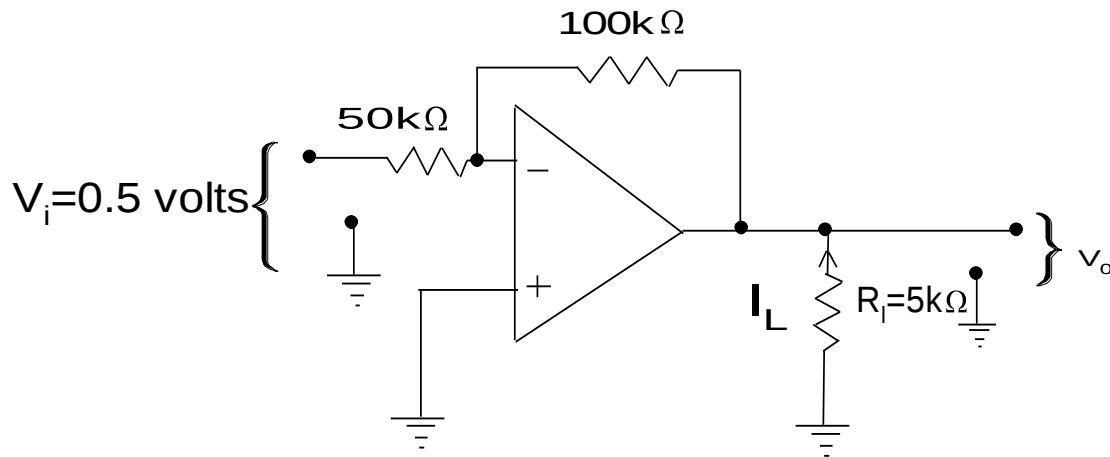1. a) Draw the circuit diagram of a subtrator using OPAMP and derive the expression for its output voltage. (4)
- b)



(6)

Calculate

- i) Voltage gain A_v .
- ii) Calculates the load Current I_L .
- iii) Output voltage.

2. a) What do you mean by slew rate of an OPAMP. (2)
- b) Explain the operation of OPAMP as integrator. From this, explain how it can act as Low pass filter. (4 + 2)
- c) What is CMRR? What is the value of CMRR for an ideal OPAMP. (2)
3. a) Explain with the help of block diagram the working principle of a negative feedback amplifier. Find out the expression for the voltage gain with feedback. (3 + 3)
- b) State the effects of negative feedback in amplifiers. (4)
4. a) Explain the operation of an OPAMP as a Schmitt trigger along with a neat circuit diagram. (3 + 1)
- b) What are the different feedback topologies? Explain with neat circuit diagram. (6)
5. a) Explain a non-inverting amplifier using OPAMP. Derive the expression for voltage gain along with neat circuit diagram. (6)
- b) Explain how can you construct a voltage follower from a non-inverting amplifier using OPAMP. Write down any two important application of voltage follower. (2 + 2)
6. a) What is virtual ground? (2)
- b) What is Barkhausen Criteria? (2)
- c) What do you mean by input bias current of OPAMP? (2)
- d) What is output offset voltage of an OPAMP? Construct a circuit which can remove the effect of output offset voltage. (2 + 2)
7. a) Give the circuit diagram of a Hart Ley oscillator and explain its operation. (2 + 4)
- b) What are the fundamental differences between class A & class B amplifier. (4)