

RAMAKRISHNA MISSION VIDYAMANDIRA

(Residential Autonomous College affiliated to University of Calcutta)

B.A./B.Sc. FIRST SEMESTER EXAMINATION, DECEMBER 2015

FIRST YEAR [BATCH 2015-18]

ELECTRONICS [Gen]

Date : 17/12/2015


Time : 11 am – 1 pm

Paper : I

Full Marks : 50

Answer **any five** questions :

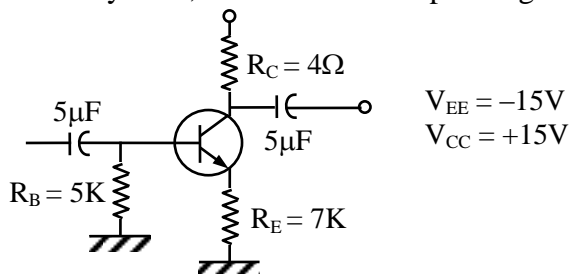1. Answer the following questions : [5×2]
 - a) Distinguish between clipping and clamping circuit.
 - b) Explain diffusion capacitance.
 - c) Establish the relation between α & β of a BJT.
 - d) What is Mass-Action Law?
 - e) What is the principle of working LED?
2. A 230 V, 60Hz voltage is applied to the primary of a 5:1 stepdown, centre tapped transformer used in a Fullwave Rectifier having a load of $900\ \Omega$. If the diode resistance and the secondary coil resistance together has a resistance of $100\ \Omega$, determine— [5×2]
 - a) dc Voltage across the load
 - b) dc current flowing through the load
 - c) dc power delivered to the load
 - d) PIV across each diode
 - e) Ripple Voltage and its frequency
3.
 - a) Why Bipolar transistors are current operated Devices? [2]
 - b) Compare between an “emitter follower” and “Darlington pair” in transistor. [2]
 - c) What is the difference between an enhancement type and a depletion type MOSFET. [2]
 - d) In the following circuit depicted below, $\beta = 99$ and $V_{BE} = 0.7V$. Calculate the quiescent values of I_B , I_C and I_E and V_{CE} . If β increases by 20%, what is the corresponding change in I_C ? [3+1]



4.
 - a) What is FET? Show two advantages of FET. [1+2]
 - b) Compare between BJT and FET. [2]
 - c) Mention the application of FET. [2]
 - d) Explain the working principle of N-channel JFET. [3]
5. What is Zener Diode? Mention the application of Zener diode. Compare between Avalanche Break Down with Zener Break Down with a neat diagram. [2+3+5]
6. Analyse the transistor current gain, input impedance, voltage gain and power gain in CE mode using h-parameter model. [10]
7.
 - a) Distinguish between Semiconductor, Conductor and Insulator using Energy band Diagram. [4]
 - b) Mention the effects of doping in formation of a semiconductor. [3]
 - c) What is PIV? Explain briefly. [2+1]
8. Write short notes on **any two** : [2×5]
 - a) Light Emitting Diode
 - b) Load Line
 - c) Pinchoff Effect
 - d) Solar Cell