

RAMAKRISHNA MISSION VIDYAMANDIRA

(Residential Autonomous College affiliated to University of Calcutta)

B.A./B.Sc. FIRST SEMESTER EXAMINATION, DECEMBER 2017

FIRST YEAR [BATCH 2017-20]

ELECTRONICS [General]

Paper : I

Date : 15/12/2017


Time : 11 am – 1 pm

Full Marks : 50


Answer **any five** questions:

5 X 10

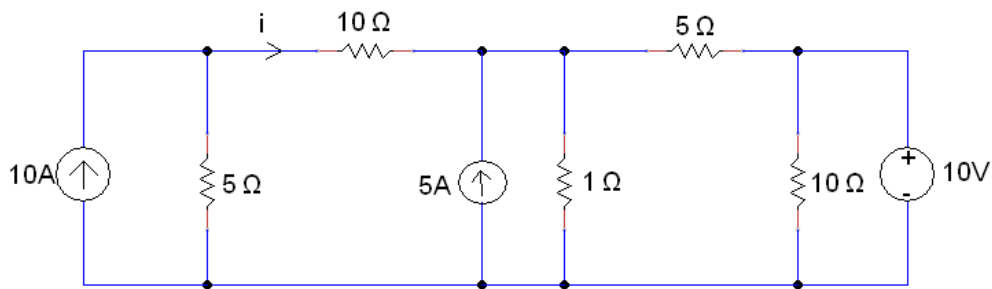
1. a) State Kirchhoff's current and voltage laws. Explain how they are equivalent to the principle of conservation of charge and conservation of energy respectively. 2+3
- b) Obtain the value of current 'i' in the following circuit: 5



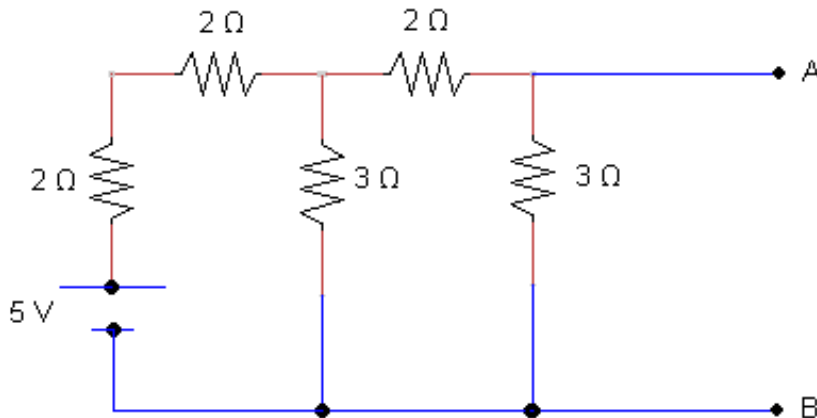2. a) State and explain Thevenin's Theorem. 3
- b) Obtain Thevenin's equivalent network for the following circuit across the point AB. 3



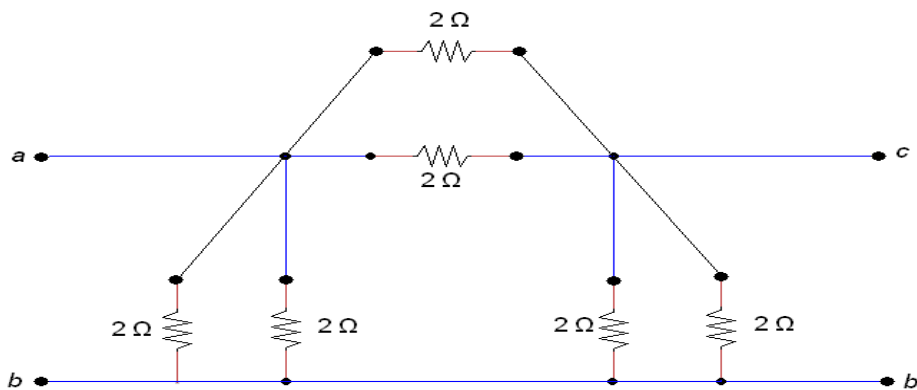- c) Obtain the equivalent T (or Y) network of the given circuit. 4



- | | | | |
|----|---|--|-------|
| 3. | a) | What do you mean by doping? | 2 |
| | b) | Define donor level and acceptor level for <i>n</i> -type and <i>p</i> -type semiconductor respectively. | 2+2 |
| | c) | What do you mean by rectifier? | 1 |
| | d) | Calculate ripple factor for centre tapped fullwave rectifier. | 3 |
| 4. | a) | Define depletion region and barrier field. | 3 |
| | b) | What do you mean by biasing? | 2 |
| | c) | Differentiate between energy band diagrams of a forward bias and reverse bias PN junction diode. | 5 |
| 5. | a) | Explain how voltage regulation can be achieved by using zener diode. | 3 |
| | b) | Find the dynamic (forward) resistance of a silicon diode when the diode voltage is 0.12 V while diode current changes below and above $I = 2.5$ mA by 5 mA. | 3 |
| | c) | A halfwave rectifier uses a junction diode of forward resistance 2Ω , a transformer of secondary winding resistance of 4Ω and a load resistance of 100Ω . If the transformer primary to secondary turns ratio is 20:1 and 220 V, 50 Hz ac is applied to the primary, find | |
| | (i) | the dc load current | |
| | (ii) | the ripple factor | |
| | (iii) | the rectification efficiency. | 4 |
| 6. | a) | Explain current components of n-p-n transistor in CB mode. | 3 |
| | b) | Draw and explain the output characteristics in CE mode of the transistor. | 4 |
| | c) | Define transistor parameters α and β . | 3 |
| 7. | a) | Draw a schematic diagram of NMOS. State its principle of operation. | 5 |
| | b) | Differentiate between depletion and enhancement type MOS. | 3 |
| | c) | State some advantages of MOS over BJT. | 2 |
| 8. | Write short notes on <u>any two</u> of the following: | | 2 X 5 |
| | a) | Bridge rectifier. | |
| | b) | Charging of a capacitor in in series C–R circuit. | |
| | c) | h-parameters | |
| | d) | JFET | |
| | e) | Maximum power transfer theorem | |

————— × —————