

RAMAKRISHNA MISSION VIDYAMANDIRA

(Residential Autonomous College affiliated to University of Calcutta)

B.A./B.Sc. FIRST SEMESTER EXAMINATION, DECEMBER 2018

FIRST YEAR [BATCH 2018-21]

ELECTRONICS [General]

Paper : I

Date : 19/12/2018



Time : 11 am – 1 pm

Full Marks : 50


Answer any five questions:

[5 × 10]

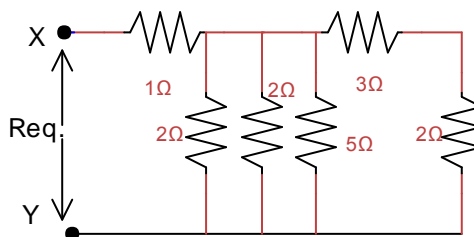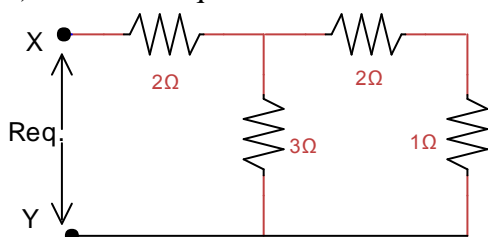1. a) A Delta network having resistances R_1 , R_2 and R_3 , is to be converted into a star network with resistance R_x , R_y and R_z . Find expressions for R_x , R_y , R_z in terms of R_1 , R_2 and R_3 . [4]
- b) Find the equivalent resistance for the given circuits: [2+2]



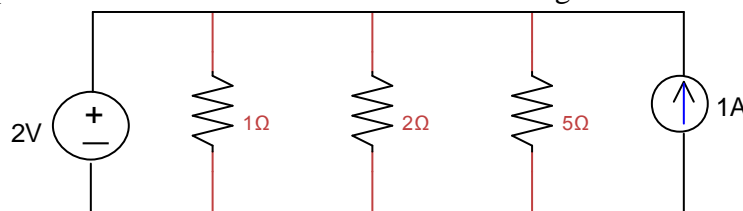- c) What do you mean by independent and dependent voltage source? Explain. [2]
2. a) State Kirchhoff's Voltage Law (KVL). Explain KVL with a neat diagram. [1+2]
 - b) What is the power absorbed in the 5Ω resistance in the given circuit: [3]



- c) State Norton's theorem. Prove that $I_N = \frac{V_{Th}}{R_{Th}}$, where, I_N is the current supplied by the Norton's equivalent current source of a given circuit, V_{Th} and R_{Th} are the Thevenin equivalent voltage source and resistance respectively of the given circuit. [1+3]
3. a) Compare forbidden band gaps of metal, insulator and semiconductor. [2]
 - b) A semiconductor has band gap energy 3.313 eV. Find the wavelength of the emitted radiation when the semiconductor is excited by a suitable excitation. [3]
 - c) Compare drift and diffusion process in semiconductors. [3]
 - d) Explain why at high temperature an extrinsic semiconductor behaves like an intrinsic one. [2]
4. a) Draw a Bridge rectifier circuit, Explain its principle of working. [4]
 - b) Define ripple factor. Prove that ripple factor,

$$\gamma = \left[\left(\frac{I_{rms}}{I_{dc}} \right)^2 - 1 \right]^{1/2}$$

where, I_{rms} and I_{dc} are the rms value and dc value of the load current respectively. [4]

- c) Explain how Zener diode can act as a voltage regulator. [2]

5. a) What is bipolar junction transistor? [1]
 b) Discuss how a transistor can be used as a current amplifier. [3]
 c) Explain the current amplification factors α and β for CB and CE configurations, respectively of a pnp transistor. Obtain a relation between them. [3]
 d) A transistor having $\alpha = 0.99$ is used in a CB amplifier. If the load resistance is $4.5 \text{ K}\Omega$ and the dynamic resistance of the emitter-base junction is 50Ω , find the voltage gain and the power gain. Also Calculate β of the transistor. [3]
6. a) When is the channel of a JFET said to be pinched off? Sketch the depletion region before and after pinch-off of the JFET. [2+2]
 b) Explain the advantages of FETs over BJTs. [3]
 c) What is the difference between an enhancement type and a depletion type MOSFET? Explain in detail. [3]
7. Write short notes on any four of the following: [4 × 2.5]
 a) Thevenin's theorem
 b) LED
 c) Avalanche breakdown.
 d) Output characteristics of BJT (CE mode)
 e) Rectification efficiency
 f) h parameters
8. Answer any five of the following: [5 × 2]
 a) 'The energy levels of an atom produce energy bands in a crystal' — Explain. [2]
 b) Draw and explain drain characteristics of MOSFET. [2]
 c) A zener diode is specified with ratings 5.5 V and 1.1 W. What is the maximum allowable current that can pass through it? [2]
 d) Prove that dynamic resistance of a diode,

$$r_{ac} = \frac{\eta}{39(I + I_s)}$$

Where, η = diode ideality factor, I_s = reverse saturation current through the diode and I = current flowing through the diode. [2]

- e) Explain charging of a capacitor in CR circuit. [2]
 f) Prove that the hybrid parameter h_{fe} is equivalent to β' , the small signal short-circuit current gain in CE mode BJT. [2]
 g) Explain briefly superposition theorem. [2]
 h) For a field-effect transistor, prove that

$$\mu = r_d g_m$$

where, μ = amplification factor, r_d = output resistance and g_m = trans-conductance. [2]

————— × —————