

RAMAKRISHNA MISSION VIDYAMANDIRA

(Residential Autonomous College affiliated to University of Calcutta)

B.A./B.Sc. SECOND SEMESTER EXAMINATION, MAY 2018

FIRST YEAR [BATCH 2017-20]

ELECTRONICS (General)

Paper : II

Date : 29/05/2018

Time : 11 am – 1 pm

Full Marks : 50

Answer any five of the following questions :

[5×10]

1. Answer any five of the following :

[5×2]

- What do you mean by transistor biasing?
- Mention four advantages of negative feedback.
- What is oscillator? Give examples for Radio frequency (RF) and Audio frequency (AF) oscillators.
- Why is CMOS called 'complementary' MOS?
- State and explain Moore's law.
- Compare oscillators and multivibrators.

2. Write short notes on any two of the following :

[2×5]

- Crystal oscillator
- TTL inverter
- Schmitt trigger
- Voltage and power amplifier

3. a) What do you mean by feedback in amplifier? What is the basic difference between positive and negative feedback? [3]

b) Mention different feedback topologies or feedback circuit configurations with their schematic circuit diagrams. [4]

c) Mention how positive feedback can be utilized for designing oscillators. [3]


4. a) What is Barkhausen criteria? [3]

b) Discuss the working principle of Wien-bridge oscillator. [5]

c) Compare Hartley and Colpitts oscillators. [2]

5. a) Design a non-inverting amplifier. Derive its voltage gain. [4]

b)

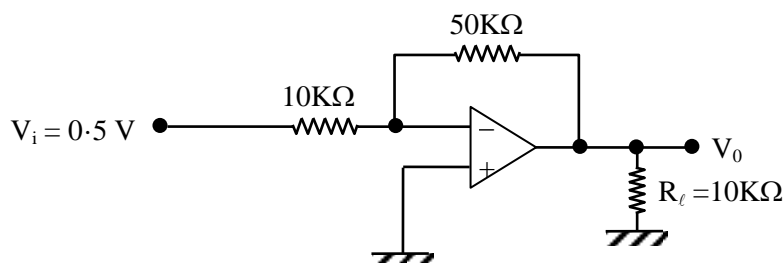

- Calculate—
- Voltage gain
 - Load Current
 - Output Voltage

[3×2]

6. a) Why power amplifiers are called large signal amplifiers? [1]

b) What are the advantages of negative feedback in power amplifiers? [3]

c) Explain the working principle of class-B Push-Pull power amplifier. [6]

7. a) Find the total harmonic distortion for an output signal having fundamental amplitude of 3.0V , the second harmonic amplitude of 1.5V , the third harmonic amplitude of 0.3V and the fourth harmonic amplitude of 0.03V . If the amplitude of the fundamental component of the output current is 2A , find the fundamental component of the output power and the total output power if $R = 10\Omega$. [5]
- b) State the working principle of a bistable multivibrator. [5]
8. a) Design a 2-input NAND gate with CMOS transistors. [3]
- b) Explain the working principle of voltage divider bias circuit with the help of its schematic diagram. Also obtain expressions of stability factors for the same. [4+3]

_____ × _____