

RAMAKRISHNA MISSION VIDYAMANDIRA

(Residential Autonomous College affiliated to University of Calcutta)

B.A./B.Sc. FOURTH SEMESTER EXAMINATION, MAY 2018

SECOND YEAR (BATCH 2016-19)

PHYSICS (General)

Date : 25/05/2018

Time : 11.00 am – 1.00 pm

Paper : IV

Full Marks : 50

[Use a separate Answer Book for each group]

Group - A

(Answer any four questions)

[4×5]

1. a) Draw the circuit diagram of a full-wave rectifier using bridge connection. [1]
b) Explain its working very clearly. What is the Peak-Inverse Voltage (PIV) of the rectifier. [3+1]
2. a) Describe the characteristics of a transistor in the CE mode of operation with a suitable circuit. [2+1]
b) Prove the relation : $\beta = \frac{\alpha}{1-\alpha}$ where α is the current gain in the CB mode and β in the CE mode of operation respectively. [2]
3. a) What is zener diode? Explain its characteristics. [1+2]
b) Breakdown voltage of a Zener diode is 4.7V and its resistance is 100Ω . It is connected to a 10V supply. Determine the current in the breakdown condition through the Zener. [2]
4. a) For the logic expression $Y = A\bar{B} + \bar{A}B$, realize this operation using NAND gate only. [3]
b) Prove the following using De Morgan's theorem.
 1. $\bar{A} \bar{B} \bar{C} + \bar{A} BC + ABC + A \bar{B} \bar{C} = \bar{B} \bar{C} + BC$
 2. $(A+BC)(B+\bar{C}A) = AB + A\bar{C} + BC$ [1+1]
5. a) Perform the following operations with binary number system using 2's complement method.
(i) $45 - 25$ (ii) $25 - 45$ (iii) $-45 - 25$ [3]
b) Given the logical equation, $Y = AB + A\bar{C} + BC$. Design a circuit using gates to realize Y. [2]
6. What is Full-Adder? Realize the Full-Adder circuit with the help of truth table. [5]

Group - B

(Answer any six questions)

[6×5]

7. a) Consider the nuclear reaction : $x + X = y + Y$. The symbols bear their usual meanings. Calculate Q-value of the reaction. [2]
b) What is mean life of a radioactive atom. Derive an expression of it. [1+2]
8. a) What do you mean by binding energy per nucleon and packing fraction. [1.5+1.5]
b) Plot a graph between packing fraction and mass number and discuss the graph. [2]
9. a) How transient equilibrium and secular equilibrium occurs in successive disintegration. [2+2]
b) Write a name of radio isotope and its use. [1]
10. a) Write down time dependent Schrodinger equation. Prove that time evolution of the state $\psi(t)$ is determined by the Hamiltonian. [1+2]
b) Normalise the wave function as defined : [2]
$$\psi(x) = Ae^{-\alpha x} \text{ for } x > 0 \text{ and}$$
$$= Ae^{\alpha x} \text{ for } x < 0$$

11. From relativistic momentum conservation show that $m = \frac{m_0}{\sqrt{1 - \frac{v^2}{c^2}}}$ where m is the mass of the moving body and m_0 is its rest mass, c is the velocity of light and v is the relative velocity of two frame. [5]
12. a) Show that in the space time interval $x^2 + y^2 + z^2 - c^2 t^2$ is invariant. [3]
 b) A radioactive nucleus of half-life $1\mu s$ moves through the laboratory at $2.7 \times 10^{10} \text{ cm/s}$. What will be its half life as measured by an observer in the laboratory? $c = 3 \times 10^{10} \text{ cm/s}$. [2]
13. a) What are the basic lattice parameters? Define a mono-clinic crystal in terms of the lattice parameters. [1+1]
 b) Write down Bragg's law for crystal diffraction. For an X-ray diffraction of wavelength 0.842 \AA the glancing angle is $8^\circ 35'$ for the first order. What will be the glancing angle for the third order? (Given $\sin(8^\circ 35') = 0.15$) [1+2]
14. An electron is trapped in an infinite square well of length $2 \times 10^{-10} \text{ m}$. In the ground state, calculate the probability of finding the particle between $x = 0$ to $x = 0.25 \times 10^{-10} \text{ m}$. [5]
15. What is Compton effect? Obtain an expression for the Compton shift. [1+4]
16. State de Broglie hypothesis. Establish Bohr's quantization condition on the basis of de Broglie's concept of matter waves. From the expression of phase velocity u of de Broglie waves i.e. $u = c \sqrt{1 + \frac{m_0^2 c^2 \lambda^2}{h^2}}$. Show that the de Broglie waves show dispersion in vacuum. [1+2+2]

_____ × _____