

**RAMAKRISHNA MISSION VIDYAMANDIRA**  
(Residential Autonomous College affiliated to University of Calcutta)

FIRST YEAR [2019-22]

B.A./B.Sc. FIRST SEMESTER (July – December) 2019  
Mid-Semester Examination, September 2019

Date : 18/09/2019

Time : 11 am – 12 noon

**COMPUTER SCIENCE (General)**

Paper: I

Full Marks : 25

**[Use a separate Answer Book for each group]**

**GROUP – A**

Answer **any one** from question nos. **1 & 2** :

(1 × 2.5)

1. Reduce the following expression using K-map:

$$F = \Pi(2, 8, 9, 10, 11, 12, 14)$$

[2.5]

2. Differentiate between the following terms:

a) Primary memory and Secondary memory.

[1.5]

b) Von Neumann Architecture and Harvard Architecture.

[1]

Answer **any two** from question nos. **3 to 5** :

(2 × 5)

3. a) Encode data bits 1101 into 7-bits even parity hamming code.

[3]

b) Subtract  $(111.111)_2$  from  $(1010.01)_2$

[2]

4. a) Using only NAND gate, implement OR gate.

[2.5]

b) Convert  $(108.32)_{10}$  to binary.

[2.5]

5. a) Why Gray code is a reflective code?

[2]

b) Perform the BCD subtraction : 109.8-92.5

[3]

**GROUP – B**

Answer **any one** from question nos. **6 and 7** :

(1 × 2.5)

6. Explain combination logic circuit.

[2.5]

7. Why is Decoder known as 'Minterm Generator'?

[2.5]

Answer **any two** from question nos. **8 to 10** :

(2 × 5)

8. a) While designing Adder, only three inputs are taken into consideration at most. Explain why.

[3]

b) What kind of Adder will you use to add two binary numbers of 4-bits each.

[2]

9. a) Implement the following expression using Multiplexer:

$$F(A, B, C, D) = \sum(1, 2, 4, 7, 6, 8, 10, 15)$$

[3]

b) What do you mean by Code Converter?

[2]

10. Design a 4-bits Magnitude Comparator.

[5]