RAMAKRISHNA MISSION VIDYAMANDIRA (Residential Autonomous College affiliated to University of Calcutta)			
FIRST YEAR [2018-21] B.A. /B.Sc. FIRST SEMESTER (January – June) 2019 Mid-Semester Examination, March 2019			
Date	e :2	26/03/2019 ELECTRONICS (General)	
Time : 11 am – 12 noon Paper. II Full Marks: 25			
Answer <u>any five</u> questions of the following: $[5 \times 5]$			
1.	a)	What is load line? State its significance.	
	b)	What do you mean by quiescent point of a transistor amplifier?	[2+2+1]
2.	a)	What is thermal runaway? How does it take place in a BJT amplifier?	
	b)	What are the factors that affect the bias stability of a transistor?	[1+2+2]
3.	a)	Compare class A,B,AB and C amplifiers.	
	b)	Draw circuit of a class B amplifier.	[3+2]
4.	a)	State advantages of negative feedback. Give one example where positive feedback	edback is
	h)	What do you mean by sampling and mixing in any feedback network?	[2+1+2]
5	a)	State Barkhausen criterion for oscillation	[_ + 1 + 2]
5.	u)	Describe the working of a Colpitts oscillator	[1+4]
6.	a)	Compare properties of practical OPAMP with that of ideal one.	[]
	b)	Define and explain CMRR.	[2+3]
7.	a)	Describe the applications of an OPAMP as a non-inverting amplifier.	
	b)	State the condition under which the non-inverting amplifier will act as a unity gain by	uffer. [3+2]
8.	Ŵr	tite a short note on any two of the following:	[2×2.5]
	a)	h parameter	
	b)	Stability factors	
	c)	Voltage sampling-voltage mixing feedback	
	d)	Virtual ground	
	e)	OPAMP as voltage comparator	

- × -