

# RAMAKRISHNA MISSION VIDYAMANDIRA

(Residential Autonomous College under University of Calcutta)

FIRST YEAR

B.A./B.SC. FIRST SEMESTER (July – December), 2012

Mid-Semester Examination, September 2012

COMPUTER SCIENCE (General)

Date : 11/09/2012

Time : 11 am – 12 noon

Paper : I

Full Marks : 25

Answer *Question No. 1* and *any two* from rest of the questions

1. Answer *any two* questions:

$2\frac{1}{2} \times 2$

a) Convert the following decimal numbers to the indicated bases:

i) 1938.257 to hexadecimal.

1

ii) 175.175 to binary.

$1\frac{1}{2}$

b) Simplify the Boolean function using K-map in sum of product:

$$F(w,x,y,z) = \Sigma(0,1,2,3,7,8,10).$$

$$+ d(w,x,y,z) = \Sigma(5,6,11,15).$$

c) What kind of coding technique is used in K-Map? Why is it used?

d) Design EOR function with minimum number of NAND Gate.

2. a) Prove the DeMorgan's theorem (i.e.  $(x+y)' = x'y'$  and  $(xy)' = x'+y'$ ).

3

b) Simplify the following Boolean expressions to a minimum number of literals (using basic theorems):

3

i)  $x' + xy + xz' + xy'z'$ .

ii)  $x'y + y'x + xy + x'y'$ .

c) Simplify the Boolean function using K-map in product of sum:

$$F(w,x,y,z) = \Sigma(0,2,5,6,7,8,10).$$

2

d) Find the 9's complement of the decimal number 12349876

2

3. Design a combinational circuit that has four inputs and one output. The inputs are represented in gray code and output is represented in binary which is equal to one when i) *all inputs are equal to one* or ii) *none of the inputs are equal to one* or iii) *number of ones in input combination are more than number of zeros.*

10

4. a) What do you mean by Full-Subtractor? Show how a Full-Adder can be converted to a Full-Subtractor circuit.

1 + 4

b) What do you mean by Universal Gate? Prove that NAND gate is a Universal Gate.

2 + 3