RAMAKRISHNA MISSION VIDYAMANDIRA (Residential Autonomous College affiliated to University of Calcutta)			
FIRST YEAR [2015-18] B.A./B.Sc. FIRST SEMESTER (July – December) 2015 Mid-Semester Examination, September 2015			
Date : 15/09/2015 COMPUTER SCIENCE (General)			
Time	e : 1	12 noon – 1 pm Paper : I	Full Marks : 25
<u>Group – A</u>			
1.	Ans a) b)	swer any one question : "Gray code is unit distance reflective code" — Justify. Minimize the following expression using Boolean algebra (mention the laws). a'bc+ab'c+abc'+abc	[2.5]
Answer <u>any one</u> of the following questions : $[1 \times 10]$			
2.	a)	Using 1's complement perform : $(101)_2 - (10)_2$	[1.5]
	b)	'8 $4 - 2 - 1$ ' code is self-complementing —Justify	[2]
	c)	Determine : $(0.01)_2 = (?)_{10}$	[1.5]
	d)	Subtract $(111.111)_2$ from $(1010.01)_2$	[2]
	e)	Following is the received codeword in 7-bit hamming code using even parity scheme. whether the received codeword has error. If it has correct it. 1011010	Check [3]
3.	a)	Simplify the following Boolean function by first finding the essential prime implicants. $F(A, B, C, D) = \Sigma(0, 2, 3, 5, 7, 8, 10, 11, 14, 15)$	[4]
	b)	Express the following Boolean function into the canonical P.O.S form $F = xy + x'z$.	[3]
	c)	What do you mean by don't care condition? Explain with example.	[3]
<u>Group – B</u>			
4.	Ans	swer any one question :	[2.5]
	a)	Draw the circuit diagram of Half- Adder. Give truth table also.	
	b)	What are asynchronous inputs in flip-flop? Explain their operation.	
Answer <u>any one</u> of the following questions : $[1 \times 10]$			
5.	a)	What do you mean by Universal gate? Explain with example.	[4]
	b)	How can you construct a 16×1 Multiplexer using two 8×1 multiplexer?	[3]
	c)	Implement the following Boolean function $F(A, B, C, D) = \Sigma(0, 1, 2, 3, 4, 8, 9, 14, 15)$ Usir 8×1 multiplexer?	ig one [3]
6.	a)	Differentiate between edge-triggered flip-flop and level-triggered flip-flop.	[2]
	b)	Realize a flip-flop using J-K flip-flop.	[3]
	C)	what is race around codition? How does master-slave flip-flop avoid it? Explain with j diagram.	[2+3]

- × —