

RAMAKRISHNA MISSION VIDYAMANDIRA

(Residential Autonomous College affiliated to University of Calcutta)

FIRST YEAR [2018-21]

B.A./B.Sc. FIRST SEMESTER (July – December) 2018

Mid-Semester Examination, September 2018

Date : 25/09/2018

COMPUTER SCIENCE (General)

Time : 12 noon – 1pm

Paper: I

Full Marks : 25

[Use a separate Answer Book for each group]

GROUP – A

Answer **any one** from question nos. 1 & 2 :

(1 × 2½)

1. Write down the characteristics of the 2's complement numbers.
2. Convert $(1199)_{10}$ to decimal and binary.

Answer **any two** from question no. 3 to 6 :

(2 × 5)

3. Determine the possible bases in the following operations:

a) $1234 + 5432 = 6666$

2½

b) $\frac{302}{20} = 12.1$

2½

4. a) Convert the following octal numbers to hexadecimal.

(i) 1762.46_8

2

(ii) 6054.263_8

2

b) Subtract $(1011)_2$ from $(10110)_2$.

1

5. a) Define BCD.

1

b) Define weighted and non-weighted codes.

1+1

c) Define reflective code with a suitable example.

2

6. a) Convert $(101010110101)_2$ into Gray Code.

2

b) Prove $A \oplus \bar{A} = 1$

1

c) State De Morgan's theorem.

2

GROUP – B

Answer **any one** from question nos. 7 & 8:

(1 × 2½)

7. "A decoder with an enable input is called a demultiplexer" – justify.
8. Differentiate between combinational logic circuit and sequential logic circuit.

Answer **any two** from question nos. 9 to 12:

(2 × 5)

9. a) Derive the characteristic equation of J-K flip-flop.

4

b) Differentiate between latch and flip-flop.

1

10. Design a 4-bit BCD-to-Excess3 code converter circuit.

11. Design a 4-input priority encoder with four inputs and three outputs including the valid output but with the truth table representing input D_0 has the highest priority and input D_3 has the lowest priority.

12. Implement a three input exclusive OR gate using a suitable multiplexer.

————— × —————