

# RAMAKRISHNA MISSION VIDYAMANDIRA

(Residential Autonomous College under University of Calcutta)

FIRST YEAR

B.A./B.SC. FIRST SEMESTER (July–December), 2012

Mid-Semester Examination, September, 2012

**ELECTRONICS (General)**

Date : 11/09/2012

Time : 11am – 12noon

Paper : I

Full Marks : 25

Answer *Question No. 1* and *any four* from rest of the questions

1. Compulsory Questions :-

5x1=5

- What do you mean by Combinational Logic Circuit ?
- What is Nibble ?
- What is the difference between Boolean Algebra & Ordinary Algebra?
- Convert  $(0.3125)_{10}$  to Binary.
- Find out 2's Complement of  $(1101011101000)_2$

2. Solve the following equations using K map Only: -  $X = BC'D + A'BC'D + ABC'D + A'BCD + ABCD$  5

3. Draw & Explain the operation of Full Adder using logic gates with Truth Table 5

4. Write Short Notes on --4 bit Binary Parallel Adder 5

5. Design a 4 bit Binary to Gray Code Converter 5

6. Design a 32:1 Mux using 16:1 Mux. 5

7. Simplify with Boolean Algebra :  $Y = A'BC + B'CD + AC + A'B'CD'$  5

8. a) State and prove De Morgan's Theorem.

b) What do you mean by Positional weighting?

$2\frac{1}{2} + 2\frac{1}{2}$