

# RAMAKRISHNA MISSION VIDYAMANDIRA

(Residential Autonomous College under University of Calcutta)

SECOND YEAR

B.A./B.SC. THIRD SEMESTER (July – December) 2014

Mid-Semester Examination, September 2014

Date : 16/09/2014

**ELECTRONICS (General)**

Time : 12 noon – 1 pm

Paper : III

Full Marks : 25

1. A class CE amplifier operates from  $V_{CC} = 20V$ , draws a no signal current of 5A and feeds a load of  $40\Omega$  through a step-up transformer of  $n_2/n_1 = 3 \cdot 16$ . Find—

- Whether the amplifier is properly matched for maximum power transfer
- maximum ac signal power output
- maximum dc power input
- Conversion efficiency at maximum signal input

[10]

**Or,**

Mention the advantages of negative feedback. With a negative feedback, an amplifier gives an output of 10V with an input of 0.5V. When the feedback is removed, it requires 0.25V input for the same output. Calculate—

- gain without feedback
- feedback fraction  $\beta$

[10]

2. Write short notes **any three** of the following :

[3×5]

- Power Amplifier and its characteristics
- Virtual Ground of OP-AMP
- Input offset Voltage & Offset Null of OP AMP
- Inverting mode gain of OP-AMP
- Feedback Amplifier and its gain.

————— × —————