RAMAKRISHNA MISSION VIDYAMANDIRA (Residential Autonomous College under University of Calcutta)				
FIRST YEAR B.A./B.Sc. SECOND SEMESTER (January – June) 2015 Mid-Semester Examination, March 2015				
Date : 19/03/2015 ELECTRONICS (General)				
Time	e : 12 noon – 1 pm	Paper : II	Full Marks : 25	
1.	What is Integrated Circuit? Mention the applications of IC.	ne advantages and disadvantages of IC. Mention	some (10)	
	Calculate the gain of Inverting Amploperational amplifier?	lifier using OP-AMP 741C. Why OP-AMP is	called (10)	
2.	2. Mention the advantages of Feed Back in Negative Mode. Calculate the overall gain of Negative			
	Feed Back Amplifier.	-	(10)	
OR				
	Define the following :-		$(4 \times 2^{1/2})$	
	i) CMRR ii)	Slew Rate		
	iii) Off-Set Null iv)	Ideal characteristics of OP-AMP.		
3.	Calculate the gain stability of an amplifie	er used in Negative mode.	(5)	

R	CAMAKRISHNA MISSION VIDYAMANDIRA (Residential Autonomous College under University of Calcutta)	A	
FIRST YEAR B.A./B.Sc. SECOND SEMESTER (January – June) 2015 Mid-Semester Examination, March 2015			
Date : 19/03/2015	ELECTRONICS (General)		
Time : 12 noon – 1 pm	Paper : II	Full Marks : 25	
1. What is Integrated	Circuit? Mention the advantages and disadvantages of IC.	Mention some	

X -

applications of IC.

<u>OR</u>

Calculate the gain of Inverting Amplifier using OP-AMP 741C. Why OP-AMP is called operational amplifier? (10)

2. Mention the advantages of Feed Back in Negative Mode. Calculate the overall gain of Negative Feed Back Amplifier.

<u>OR</u>

Define the following :-

- CMRR ii) Slew Rate i)
- iii) Off-Set Null iv) Ideal characteristics of OP-AMP.
- 3. Calculate the gain stability of an amplifier used in Negative mode.

- × —

 $(4 \times 2^{1/2})$

(10)

(5)

(10)