

RAMAKRISHNA MISSION VIDYAMANDIRA

(Residential Autonomous College affiliated to University of Calcutta)

FIRST YEAR [BATCH 2015-18]

B.A./B.Sc. SECOND SEMESTER (January – June) 2016

Mid-Semester Examination, March 2016

Date : 18/03/2016

ELECTRONICS (General)

Time : 12 noon – 1 pm

Paper : II

Full Marks : 25

1. Answer any five questions :

[5×3]

- a) What is the difference between current and voltage feedback?
- b) Why voltage series feedback is most commonly used in Cascaded amplifiers?
- c) An amplifier with voltage gain of 60db uses $\frac{1}{20}$ of its output in negative feedback. Calculate the gain with feedback in db.
- d) What is the effect of removing bypass capacitor across the emitter resistor in case of a CE amplifier?
- e) Why are L-C resonant circuit impractical at audio frequencies?
- f) What are the Barkhausen conditions of oscillations?
- g) Why Clapp oscillator is preferred over the Colpitt's oscillator?
- h) Why is Crystal oscillator used in Communication transmitters and receivers?

Answer any one question from question no. 2&3 :

[1×10]

- 2. Describe the operation of Hartley oscillator with a neat sketch. [10]
- 3. a) A negative feedback of $\beta = 0.002$ is applied to an amplifier of gain 1,000. Calculate the change in overall gain of the feedback amplifier if the internal amplifier is subjected to a gain reduced of 15%. [5]
- b) Voltage gain of an amplifier without feedback is 60db. It decreases to 40db with feedback. Calculate the feedback factor. [5]

_____ × _____