

**RAMAKRISHNA MISSION VIDYAMANDIRA**  
(Residential Autonomous College affiliated to University of Calcutta)

SECOND YEAR [2016-19]  
B.A./B.Sc. THIRD SEMESTER (July – December) 2017  
Mid-Semester Examination, September 2017

Date : 15/09/2017

**ELECTRONICS (General)**

Time : 12 noon – 1 pm

Paper : III

Full Marks : 25

Answer **any five** of the following questions :

[5×5]

1. State some sources of error while measurement of a parameter. The expected value of current passing through a resistor is 90mA. However, the measurement gives a value of 85mA. Calculate—  
(i) absolute error, (ii) percentage error, (iii) relative accuracy and (iv) percentage accuracy. [2+3]
2. What is CRT? Mention some characteristics of a CRT. [2+3]
3. Draw a schematic block diagram of a CRO and indicate all the components. [5]
4. How is a signal traced using a CRO? Explain, how frequency and phase can be determined with the help of a CRO. [2+3]
5. State basic characteristics of TTL and ECL logic families respectively. [5]
6. Mention advantages of CMOS technology over the NMOS technology. Draw and explain an NMOS inverter switch. [2+3]
7. Draw and explain the operation of a 3-input NOR using CMOS technology. Explain how it can be converted into a 3-input OR gate. [3+2]
8. State some important capabilities of VHDL. What do you mean by entity? Give the syntax of entity declaration for a 2×4 decoder circuit. [2+1+2]

————— × —————