

RAMAKRISHNA MISSION VIDYAMANDIRA

(Residential Autonomous College under University of Calcutta)

SECOND YEAR

B.A./B.Sc. FOURTH SEMESTER (January – June) 2015

Mid-Semester Examination, March 2015

Date : 21/03/2015

PHYSICS (General)

Time : 12 noon – 1 pm

Paper : IV

Full Marks : 25

Answer any five questions :

[5×5]

1. Draw I-V characteristic of P-N junction diode and explain. What is Zener breakdown? [3+2]
2. Find the relation between α and β . Define α and β . [3+2]
3. Explain with a diagram an universal gate. Which one is an universal gate NAND or NOR. [4+1]
4. State, explain and prove De Morgan's theorem using truth table. [5]
5. a) $(11001)_2 - (10001)_2$ make this subtraction by 1's compliment method. [4]
b) Make 2's compliment of $(1101)_2$ [1]
6. a) $(10.25)_{10} = (X)_2$ find the value of X [2.5]
b) $(6.75)_{10} = (Y)_2$ find the value of Y. [2.5]

_____ × _____

RAMAKRISHNA MISSION VIDYAMANDIRA

(Residential Autonomous College under University of Calcutta)

SECOND YEAR

B.A./B.Sc. FOURTH SEMESTER (January – June) 2015

Mid-Semester Examination, March 2015

Date : 21/03/2015

PHYSICS (General)

Time : 12 noon – 1 pm

Paper : IV

Full Marks : 25

Answer any five questions :

[5×5]

1. Draw I-V characteristic of P-N junction diode and explain. What is Zener breakdown? [3+2]
2. Find the relation between α and β . Define α and β . [3+2]
3. Explain with a diagram an universal gate. Which one is an universal gate NAND or NOR. [4+1]
4. State, explain and prove De Morgan's theorem using truth table. [5]
5. a) $(11001)_2 - (10001)_2$ make this subtraction by 1's compliment method. [4]
b) Make 2's compliment of $(1101)_2$ [1]
6. a) $(10.25)_{10} = (X)_2$ find the value of X [2.5]
b) $(6.75)_{10} = (Y)_2$ find the value of Y. [2.5]

_____ × _____