

# RAMAKRISHNA MISSION VIDYAMANDIRA

(Residential Autonomous College under University of Calcutta)

SECOND YEAR

B.A./B.Sc. FOURTH SEMESTER (January – June) 2015

Mid-Semester Examination, March 2015

Date : 18/03/2015

Time : 11 am – 1 pm

PHYSICS (Honours)

Paper : IV

Full Marks : 50


[Use a separate answer book for each group]

## Group – A

Answer any three questions :

[3×10]

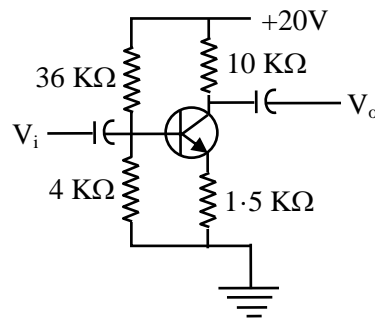1. a) Draw circuit diagram of an n-p-n transistor in CE mode from drawing output characteristics and explain how the two constants  $\alpha$  and  $\beta$  can be obtained from these curves. [1+2]
- b) What do you mean by thermal stability of a transistor? Show that the thermal stability of a collector to base bias circuit is better than that of fixed bias circuit. [1+3]
- c) Find the collector current, base current and collector emitter voltage of the following circuit. [3]



Given,  $\beta = 150$  and  $I_{CBO}$  negligible.

2. a) Define four h-parameters of a small signal low frequency transistor. [2]
- b) Draw an equivalent circuit of transistor using these parameters. Simplify the circuit with proper assumptions. Determine the voltage gain and input impedance. [1+1+3]
- c) A bypass capacitor is connected across the emitter resistance  $1.5\text{ K}\Omega$  in the circuit of previous question. Calculate the voltage gain and current gain. Given  $h_{fe} = 140$  and  $h_{ie} = 1100\ \Omega$ . [3]
3. Find the condition of balance of an AC bridge. Give the circuit diagram of Anderson Bridge. Give its condition of balance and obtains an expression for inductance. [2+2+2+4]
4. a) Draw a circuit diagram of current mirror. Design it by using similar transistors and is to be provide a  $0.5\text{ A}$  current with  $V_{CC} = 10\text{ V}$ ,  $B_f = \beta_c = 125$ . Determine the value of R. [2+3]
- b) In a common emitter amplifier circuit, a capacitor is connected between emitter and ground. Find the expression for lower frequency response of He amplifier. [5]

Answer any one question :

[1×5]

5. Draw the circuit diagram of a fullwave rectifier and explain its operation. Also calculate the ripple factor. [1+2+2]
6. Find out an expression for the impedance of parallel resonance circuit. Determine how does the current vary with the variation of capacitance in the circuit. [3+2]

## Group – B

**Answer any one question :**

[1×10]

7. a) An ideal gas Carnot engine is made to operate as a refrigerator. Explain its operation with the help of an enthalpy-entropy diagram. Find a relation between coefficient of performance (COP) of the refrigerator and the efficiency of the Carnot engine. [4]
- b) In a cold country (environment temperature  $-13^{\circ}\text{C}$ ), to keep the inside of the room at a comfortable temperature of  $17^{\circ}\text{C}$ , a heat pump is installed instead of a room heater. Find the power of a heat pump assuming maximum efficiency. Assume that heat loss from the room is 435 W. [4]
- c) Write down the Kelvin-Planck Statement and the Clausius statement of the second law of thermodynamics. [2]
8. a) Derive the third TdS equation :  $TdS = C_v \left( \frac{\partial T}{\partial P} \right)_v dP + C_p \left( \frac{\partial T}{\partial V} \right)_p dV = \frac{C_v \chi_T}{\beta} dP + \frac{C_p}{\beta V} dV$   
where  $\chi_T$  and  $\beta$  are isothermal compressibility and volume expansivity respectively. [3+2]
- b) Prove that Maxwell relation  $\left( \frac{\partial S}{\partial V} \right)_T = \left( \frac{\partial P}{\partial T} \right)_v$  Hence show that  $\left( \frac{\partial C_v}{\partial V} \right)_T = T \left( \frac{\partial^2 P}{\partial T^2} \right)_v$ . Find the value of  $\left( \frac{\partial C_v}{\partial V} \right)_T$  for a vander Waals' gas. [2+2+1]

**Answer any one question :**

[1×5]

9. State Clausius theorem.  
Show that in any irreversible process entropy change of the universe is always positive. [1+4]
10. Show that  $C_p - C_v = T \left( \frac{\partial P}{\partial T} \right)_v \left( \frac{\partial V}{\partial T} \right)_p$ . Find the value of  $C_p - C_v$  for a van der Waals' gas under suitable approximation. [2+3]

\_\_\_\_\_ × \_\_\_\_\_